

# Class 12 Physics

## Chapter 7 – Alternating Current

Notes By - The Conclusion Daily

---

### 7.1 Introduction

- In **DC (Direct Current)** circuits → current is constant with time.
  - In **AC (Alternating Current)** → current changes **magnitude and direction** periodically.
  - AC is widely used because it is easy to **generate, transmit, and transform**.
- 

### 7.2 Representation of AC

Let instantaneous current be:

$$i = i_0 \sin(\omega t)$$

where

- $i_0$  = peak (maximum) current
- $\omega$  = angular frequency =  $2\pi f$
- $f$  = frequency (Hz)
- $T = \frac{1}{f}$  = time period

**AC voltage:**

$$v = v_0 \sin(\omega t)$$

**Graph:** Sinusoidal wave, positive half-cycle followed by negative half-cycle.

---

### 7.3 Peak and RMS Values

- **Peak (maximum) value:**  $i_0, v_0$

- **Mean value (average over half cycle):**

$$i_{mean} = \frac{2}{\pi} i_0$$

- **Root Mean Square (RMS) value:**

$$i_{rms} = \frac{i_0}{\sqrt{2}}, \quad v_{rms} = \frac{v_0}{\sqrt{2}}$$

RMS value of AC = value of DC that produces the same heating effect.

## 7.4 AC through a Resistor

For resistor RRR,

$$i_0 = \frac{v_0}{R} \sin(\omega t)$$

- Current and voltage are **in phase**.
- Instantaneous power:

$$p = vi = \frac{v_0^2}{R} \sin^2(\omega t)$$

- Average power over full cycle:

$$P_{avg} = \frac{v_0^2}{2R} = I_{rms}^2 R$$

## 7.5 AC through a Pure Inductor

For inductor L:

$$v = L \frac{di}{dt}$$

If  $v = v_0 \sin(\omega t)$ :

$$i = \frac{v_0}{\omega L} \sin(\omega t - \frac{\pi}{2})$$

- Current **lags** voltage by **90°**.
- **Inductive reactance:**

$$X_L = \omega L = 2\pi fL$$

- **Average power = 0** (as current lags by 90°).

## 7.6 AC through a Pure Capacitor

For capacitor C:

$$q = Cv \Rightarrow i = C \frac{dv}{dt}$$

If  $v = v_0 \sin(\omega t)$ :

$$i = \omega C v_0 \sin(\omega t + \frac{\pi}{2})$$

- Current **leads** voltage by **90°**.
- **Capacitive reactance:**

$$X_C = \frac{1}{\omega C}$$

- **Average power = 0.**

## 7.7 AC through an LCR Series Circuit

A resistor (R), inductor (L), and capacitor (C) connected in series to AC source

$$v = v_0 \sin(\omega t)$$

**Net impedance:**

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

**Current amplitude:**

$$i_0 = \frac{v_0}{Z}$$

**Phase angle ( $\phi$ ):**

$$\tan\phi = \frac{X_L - X_C}{R}$$

- If  $X_L > X_C$ : current **lags** voltage.
- If  $X_L < X_C$ : current **leads** voltage.

**Instantaneous current:**

$$i = i_0 \sin(\omega t - \phi)$$

**Average power:**

$$P = V_{rms} I_{rms} \cos \phi$$

where  $\cos \phi =$  **power factor**.

---

## 7.8 Resonance in LCR Circuit

Resonance occurs when inductive reactance = capacitive reactance:

$$\begin{aligned} X_L &= X_C \Rightarrow \omega L = \frac{1}{\omega C} \\ \Rightarrow \omega_0 &= \frac{1}{\sqrt{LC}} \end{aligned}$$

At resonance:

- Impedance  $Z = R$  (minimum)
  - Current is maximum:  $I_0 = \frac{v_0}{R}$
  - Voltage and current are in phase.
- 

## 7.9 Power in AC Circuit

Instantaneous power:

$$p = vi = v_0 i_0 \sin(\omega t) \sin(\omega t - \phi)$$

Average over full cycle:

$$P = V_{rms} I_{rms} \cos \phi$$

$\cos \phi = \text{Power factor}$

- $\phi$  = phase difference between voltage & current.

**Special cases:**

| Circuit | Phase ( $\phi$ ) | Power factor ( $\cos \phi$ ) | Average Power |
|---------|------------------|------------------------------|---------------|
| Pure R  | $0^\circ$        | 1                            | Maximum       |
| Pure L  | $90^\circ$       | 0                            | Zero          |
| Pure C  | $90^\circ$       | 0                            | Zero          |

## 7.10 LC Oscillations

When a charged capacitor is connected to an inductor, energy oscillates between electric & magnetic forms.

**At any instant:**

$$\frac{q^2}{2C} + \frac{1}{2}Li^2 = \text{constant}$$

**Natural frequency:**

$$\omega = \frac{1}{\sqrt{LC}}, \quad f = \frac{1}{2\pi\sqrt{LC}}$$

Energy exchange:

- At  $t = 0 \rightarrow$  all energy electric (capacitor charged).
- At  $t = T/4 \rightarrow$  all energy magnetic (inductor current max).

## 7.11 Transformers

**Principle:**

Based on **mutual induction** — varying current in primary coil induces emf in secondary coil.

$$\frac{V_s}{V_p} = \frac{N_s}{N_p} = k$$

where

$V_s, V_p$  = secondary and primary voltages

$N_s, N_p$  = number of turns

$k$  = turn ratio

**Power (ideal transformer):**

$$V_p I_p = V_s I_s$$

**Types:**

- Step-up:  $N_s > N_p$  (voltage increases)
- Step-down:  $N_s < N_p$  (voltage decreases)

**Losses:**

Eddy currents, hysteresis, flux leakage, resistance of windings.

## 7.12 Key Formula Summary

| Concept               | Formula                             | Description               |
|-----------------------|-------------------------------------|---------------------------|
| Instantaneous current | $i = i_o \sin(\omega t)$            | Varies sinusoidally       |
| RMS value             | $I_{rms} = \frac{I_o}{\sqrt{2}}$    | Heating equivalent        |
| Mean current          | $I_{mean} = \frac{2I_o}{\pi}$       | Over half cycle           |
| Inductive reactance   | $X_L = \omega L$                    | Opposition by inductor    |
| Capacitive reactance  | $X_C = \frac{1}{\omega C}$          | Opposition by capacitor   |
| Impedance             | $Z = \sqrt{R^2 + (X_L - X_C)^2}$    | Total opposition          |
| Phase angle           | $\tan \phi = \frac{(X_L - X_C)}{R}$ | Lag/lead measure          |
| Resonant frequency    | $\omega_0 = \frac{1}{\sqrt{LC}}$    | Maximum current condition |
| Average power         | $P = V_{rms} I_{rms} \cos \phi$     | True power                |
| Transformer ratio     | $\frac{V_s}{V_p} = \frac{N_s}{N_p}$ | Step-up/down relation     |

LC frequency

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Natural oscillation

### 7.13 Quick Recap

- **AC = Alternating current** changing with time.
- **R, L, C** show resistance, reactance, and phase difference.
- **Resonance:**  $X_L = X_C$ , current maximum.
- **Power factor ( $\cos\phi$ ):** efficiency indicator.
- **Transformer:** changes AC voltage using mutual induction.
- **LC circuit:** oscillates naturally with frequency  $\frac{1}{2\pi\sqrt{LC}}$ .

THE  
CONCLUSION  
DAILY

"Hope & faith"

